

Physik und Systemwissenschaft

Test, November 2008

Erstes Semester WI08



Verhalten eines Zwei-Tank-Modells


In der Figur ist ein elektrischer Stromkreis abgebildet. Widerstands-werte und Kapazitäten sind konstant. Separate ausgemessen wurde der erste Kondensator; seine Kapazität beträgt $C_1 = 1.0 \cdot 10^{-4} \text{ F}$.

Der Stromkreis soll hydraulisch modelliert werden. Rechnungen sind aber für den elektrischen Fall durchzuführen.

Anfangs ist der erste Kondensator geladen, der zweite nicht. Zum Zeitpunkt $t = 0 \text{ s}$ schliesst man den ersten Schalter (S_1), der zweite bleibt offen. Das Diagramm zeigt die elektrische Spannung über dem ersten Kondensator. Auf der Rückseite ist eine Vergrösserung abgedruckt.

- Skizzieren Sie ein hydraulisches System, das dem elektrischen entspricht. Erklären und beschriften Sie Ihre Skizze.
- Skizzieren Sie das Diagramm (Flow Chart) eines systemdynamischen Modells für das *hydraulische* System. Benutzen Sie für die Beschriftung die selben Symbole für die Größen wie in Ihrer Zeichnung.
- Formulieren Sie alle Gleichungen für das *hydraulische* Modell.
- Skizzieren Sie den Verlauf der Spannung für den zweiten Kondensator für $0 \leq t \leq 40 \text{ s}$ im vergrösserten Diagramm auf Seite 2, und erklären Sie Ihre Antwort.
- Bestimmen Sie die Kapazität des zweiten Kondensators. Erklären Sie Ihre Rechnung.
- Zeigen Sie, wie man den Widerstand des Widerstandselementes zwischen den beiden Kondensatoren bestimmt (Sie sollten $10^5 \Omega$ erhalten).
- Zum Zeitpunkt $t = 40 \text{ s}$ wird der zweite Schalter geschlossen (der erste bleibt geschlossen). Wie gross werden die beiden Ströme und die Änderungsraten der Spannungen über den beiden Kondensatoren gleich nach 40 s sein? Der Widerstandswert des zweiten Widerstandes ist gleich dem des ersten.
- Skizzieren Sie den Verlauf der Spannungen über den beiden Kondensatoren bis 80 s im beiliegenden Diagramm. Erklären Sie Ihre Lösung.

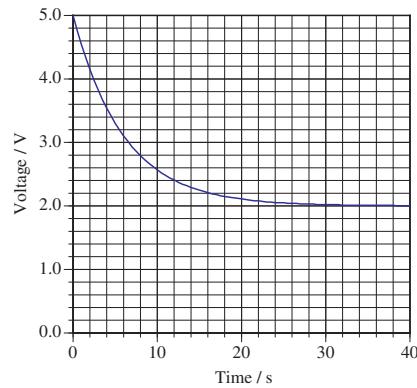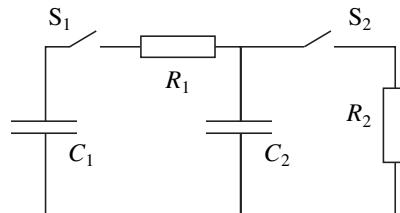


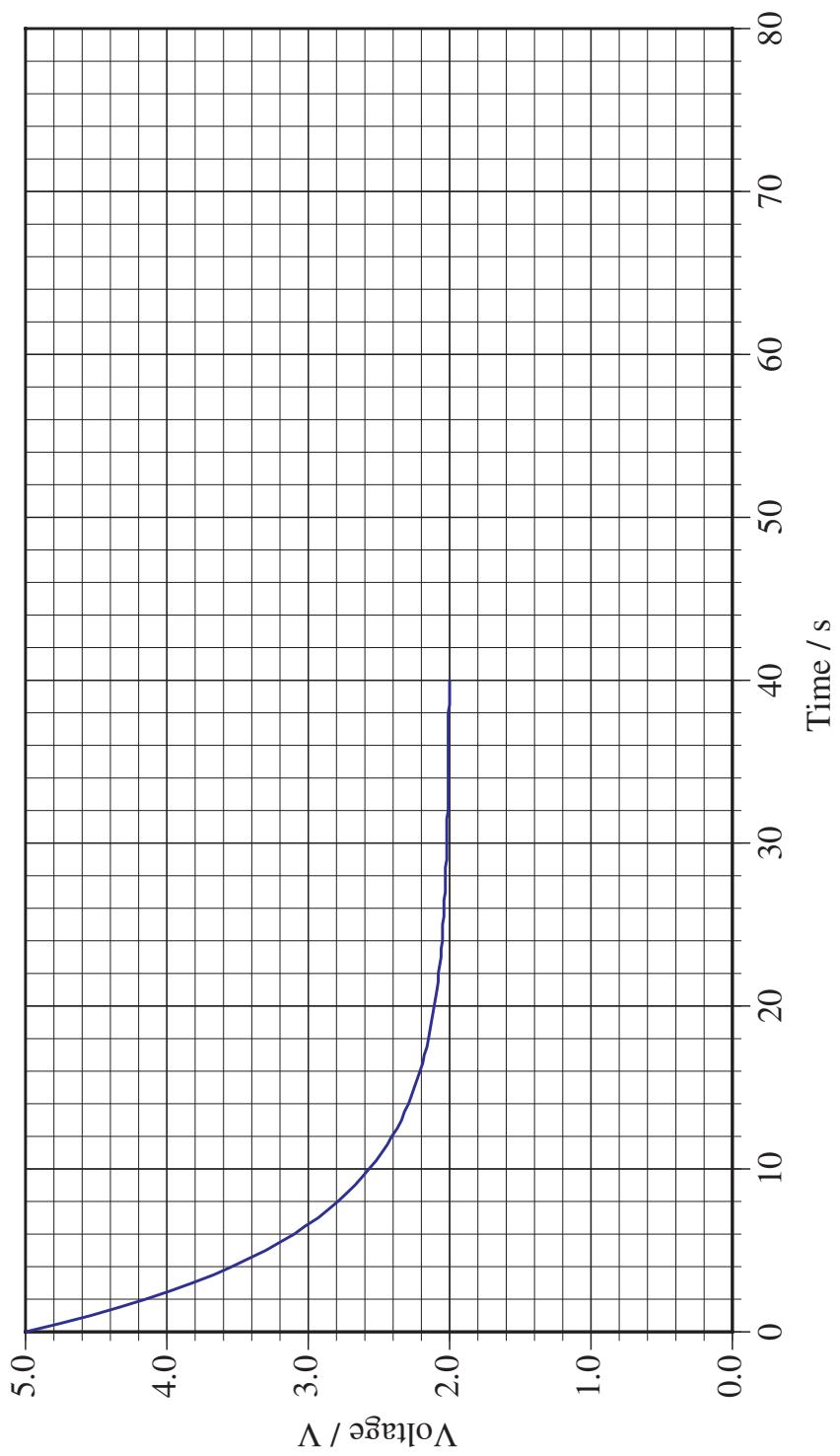

Solutions

Model of windkessel pump

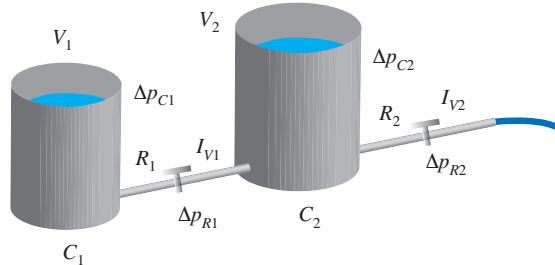- a. Two tanks connected by pipe, additional pipe for outflow, valves for each pipe. Two volumes, two flows. Pressure differences for fluid in tanks and for flows through pipes.




b. c.


```

dV1(t)/dt = - IV1
INIT V1 = C1*p1_init
dV2(t)/dt = IV1 - IV2
INIT V2 = C2*p2_init
IV1 = delta_pR_1/R1
IV2 = IF (TIME > 50) THEN
    delta_pR_2/R2 ELSE 0
delta_pC_1 = V1/C1
delta_pC_2 = V2/C2
delta_pR_1 = delta_pC_1-delta_pC_2
delta_pR_2 = delta_pC_2

```

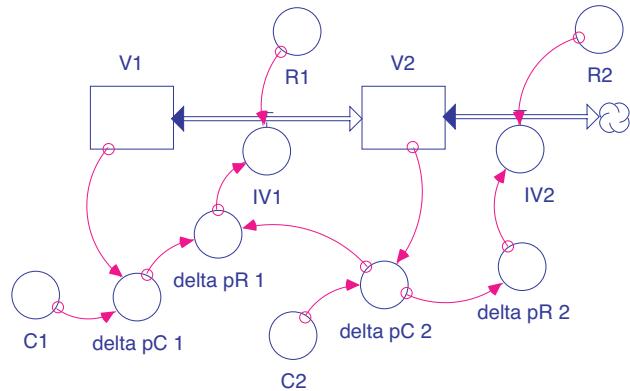

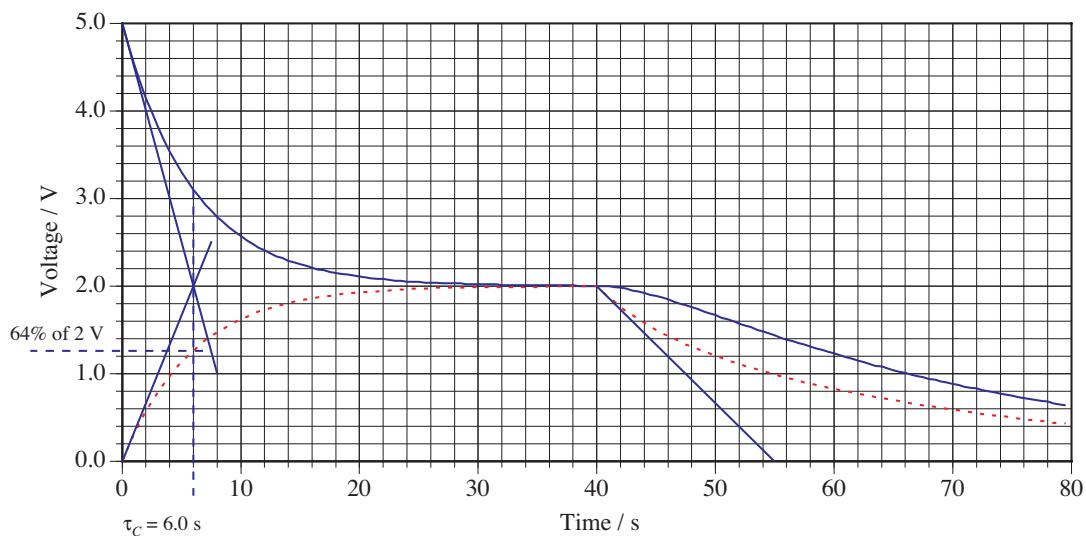- d. The voltage UC2 of the second capacitor starts at zero and mirrors the curve of UC1. It will reach a value of 2.0 V. The speed of change is determined by the time constant which can be measured from the curve for UC1 (we get $\tau_C = 6.0 \text{ s}$).



- e. Charge flows from C1 to C2 without flowing out. Therefore, the total charge of the two capacitors stays constant whereas the voltages equilibrate:

$$\begin{aligned}Q_{1,\text{init}} &= Q_{1,\text{final}} + Q_{2,\text{final}} \\C_1 U_{C1,\text{init}} &= C_1 U_{C1,\text{final}} + C_2 U_{C2,\text{final}} \\C_2 = \frac{C_1 U_{C1,\text{init}} - C_1 U_{C1,\text{final}}}{U_{C2,\text{final}}} &= \frac{1.0 \cdot 10^{-4} \cdot 5.0 - 1.0 \cdot 10^{-4} \cdot 2.0}{2.0} \text{ F} = 1.5 \cdot 10^{-4} \text{ F}\end{aligned}$$

- f. Use the time constant to determine the rate of change of UC1 at $t = 0$ s, from that determine the rate of change of Q1 which is equal to IQ1, which is used to determine R1:

$$\begin{aligned}\left. \frac{dU_{C1}}{dt} \right|_{t=0} &= \frac{U_{C1}(\tau_c) - U_{C1}(0)}{\tau_c} = \frac{2.0 - 5.0}{6.0} \text{ V} = -0.50 \frac{\text{V}}{\text{s}} \\\left. \frac{dQ_1}{dt} \right|_{t=0} &= C_1 \left. \frac{dU_{C1}}{dt} \right|_{t=0} = 1.0 \cdot 10^{-4} (-0.50) \frac{\text{C}}{\text{s}} = -0.50 \cdot 10^{-4} \frac{\text{C}}{\text{s}} \\|I_{V1}(0)| &= \left| \left. \frac{dQ_1}{dt} \right|_{t=0} \right| = 0.50 \cdot 10^{-4} \text{ A} \\R_1 &= \frac{|U_{C1}(0) - 0|}{|I_{V1}(0)|} = \frac{5.0}{0.50 \cdot 10^{-4}} \Omega = 1.0 \cdot 10^5 \Omega\end{aligned}$$

g.

$$\begin{aligned}|I_{V1}(40)| &= \frac{|U_{C1}(40) - U_{C2}(40)|}{R_1} = 0 \text{ A} \\|I_{V2}(40)| &= \frac{|U_{C2}(40)|}{R_2} = \frac{2.0}{1.0 \cdot 10^5} = 2.0 \cdot 10^{-5} \text{ A} \\\left. \frac{dU_{C1}}{dt} \right|_{t=40} &= 0 \frac{\text{V}}{\text{s}} \\\left. \frac{dU_{C2}}{dt} \right|_{t=40} &= \frac{1}{C_2} \left. \frac{dQ_2}{dt} \right|_{t=40} = \frac{1}{C_2} (I_{Q1} - I_{Q2}) = \frac{1}{C_2} \left(0 - \frac{U_{C2}(40)}{R_2} \right) \\&= \frac{1}{1.5 \cdot 10^{-4}} \left(0 - \frac{2}{1.0 \cdot 10^5} \right) \frac{\text{V}}{\text{s}} = -0.133 \frac{\text{V}}{\text{s}}\end{aligned}$$

- h. See the graph on the previous page. The beginning of the function at $t = 40$ s can be constructed from the knowledge of the rates of changes of voltages (the first curve starts horizontally, the second has a slope according to -0.133 V/s). After that, UC1 must remain above UC2, the difference is determined by the resistances. The precise runs of the functions is difficult to determine by hand. (There is one indication: If we combine the two capacitors without a resistor between them, we get $C_{\text{tot}} = 2.5 \cdot 10^{-4} \text{ F}$. With $R_2 = 10^5 \Omega$, we have a time constant for discharging of 25 s. This is a useful estimate for UC2.)